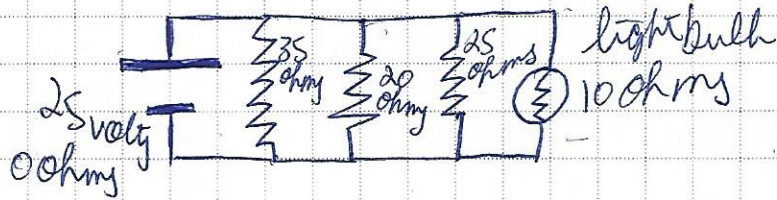


PHEt Circuit Simulation Calculations

Calculate total voltage, resistance, and current:



total voltage $V_T = 25$ volts

voltage is same across each component of a parallel circuit

total resistance $R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}}$ ohms

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \text{ ohms} = \frac{1}{\frac{1}{35} + \frac{1}{20} + \frac{1}{25} + \frac{1}{10}} \text{ ohms}$$

$$= 4.5751633 \text{ ohms} \approx \boxed{4.5752 \text{ ohms}}$$

total current $I_T = \frac{V_T}{R_T} \text{ amps} = \frac{25}{4.5752} = 5.464242 \text{ amps}$

$$\approx \boxed{5.4642 \text{ amps}}$$

DESIGNED BY:

Suraja
Reet

DATE

2/29/16

DATE

2/29/16

**PROPRIETARY
INFORMATION**

All information is the property of
and solely owned by the Designer.